

Full Name: Orkun İbrahim Kök

Department: EEE

Course Code: EEE313

Section: 02

Experiment Number: 04

Date: 23.04.2024

## Lab 4 Preliminary Report

### Introduction

The purpose of this experiment is designing a two-stage RC coupled amplifier with feedback. For amplification, BJT or MOS transistors will be used. Design specifications are given below.

Specifications:

- Source impedance:  $500\Omega$
- Load impedance:  $47\Omega$
- Voltage Gain:  $20\text{ dB} \pm 0.5\text{ dB}$
- Bandwidth ( $-3\text{ dB}$ ): at least  $5\text{ KHz}$  to  $5\text{ MHz}$
- Supply voltage:  $12\text{ V}$  (single supply)
- Maximum current consumption:  $70\text{ mA}$  from the supply voltage
- Undistorted peak-to-peak output voltage:  $2\text{ Vpp}$  at  $500\text{ KHz}$ .
- Distortion at the output: Harmonics less than  $-30\text{ dBc}$  at  $500\text{ KHz}$   $2\text{ Vpp}$  output voltage (the difference between the fundamental and the highest harmonic in FFT window)

### Methodology

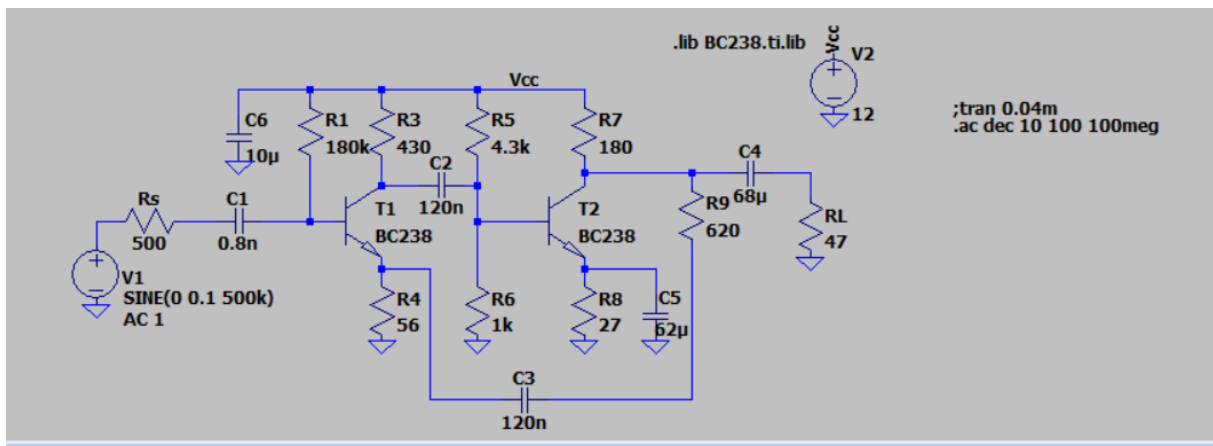


Fig. 1: Circuit Schematic

I used two BC238 BJT's in my design. I choose  $T_1$  collector current as 15mA and  $T_2$  collector current as 50mA. The sum is less than 70mA. To make voltage across R4 and R8 equals to 1V, calculations are made according to Eqn. 1.

$$V = \frac{I}{R}$$

$$R = \frac{1}{I_c} \quad (\text{Eqn. 1})$$

R4 value is calculated as 56Ω and R8 value is calculated as 27Ω. A small adjustment is done on R4 to obtain desired results.

For choosing value of R1 resistor, I solved the DC analysis of T1, assuming  $V_{BE} = 0.7V$ . From there,  $R1 = 137k\Omega$ , I changed it to 180kΩ to make the current less than 70mA.

According to specifications, current across R5 is 1/20 of collector current of T2.  $I_{R5} = 2.5mA$ . Again performing DC analysis while assuming  $V_{BE} = 0.7V$ , R5 value is found as 4120Ω, I used 4.3kΩ in my design. I choose R6 value as 1kΩ to get 50mA as the collector current of the T2 transistor.

However, when I make R9/R4 ratio as 10, which is equal to 20dB, I get 20dB in small signal analysis, but in transient analysis, I get 1V pk-pk while the input is 0.1V pk-pk.

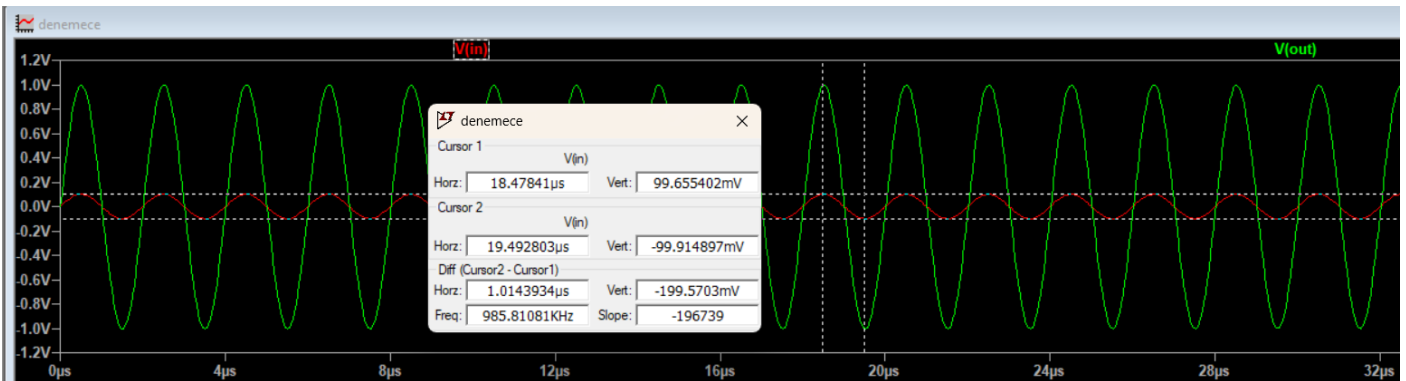


Fig. 2: Vout vs Vin at 500kHz

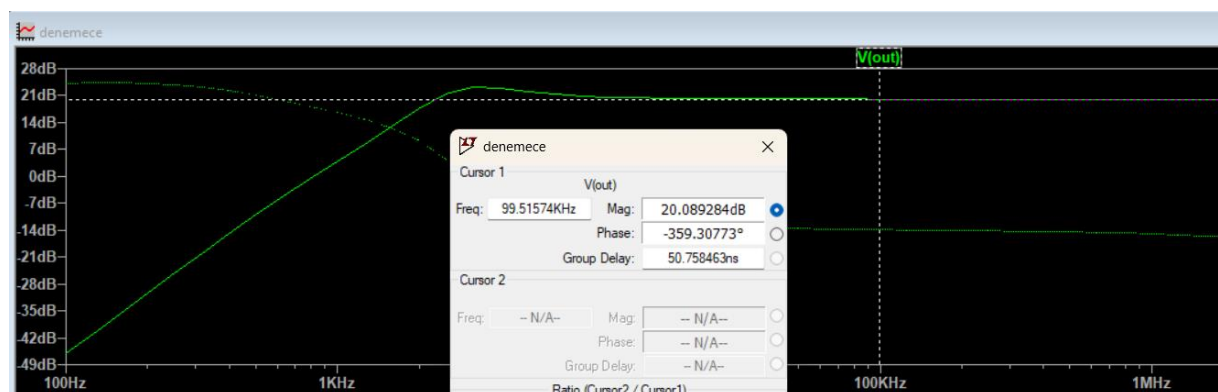


Fig. 3: 20dB gain at output

R9 value is still chosen as 620.  $R9/R4 = 11$ .

Eqn. 2 is the formula for DC-block capacitors.

$$f = \frac{1}{2\pi RC} \quad (\text{Eqn. 2})$$

Using this formula, below given the values of capacitors.

$C1 = 0.8\text{nF}$

$C2 = 120\text{nF}$

$C3 = 120\text{nF}$

$C4 = 68\mu\text{F}$

$C5 = 62\mu\text{F}$

$C6 = 10\mu\text{F}$

To get the maximum values for R3 and R7, I assumed  $V_{CE} = 0.2\text{V}$  and again performed DC analysis for both T1 and T2 transistors. After doing the calculation, R3 found as  $430\Omega$  and R7 found as  $180\Omega$ .

## Analysis

### First Specification:

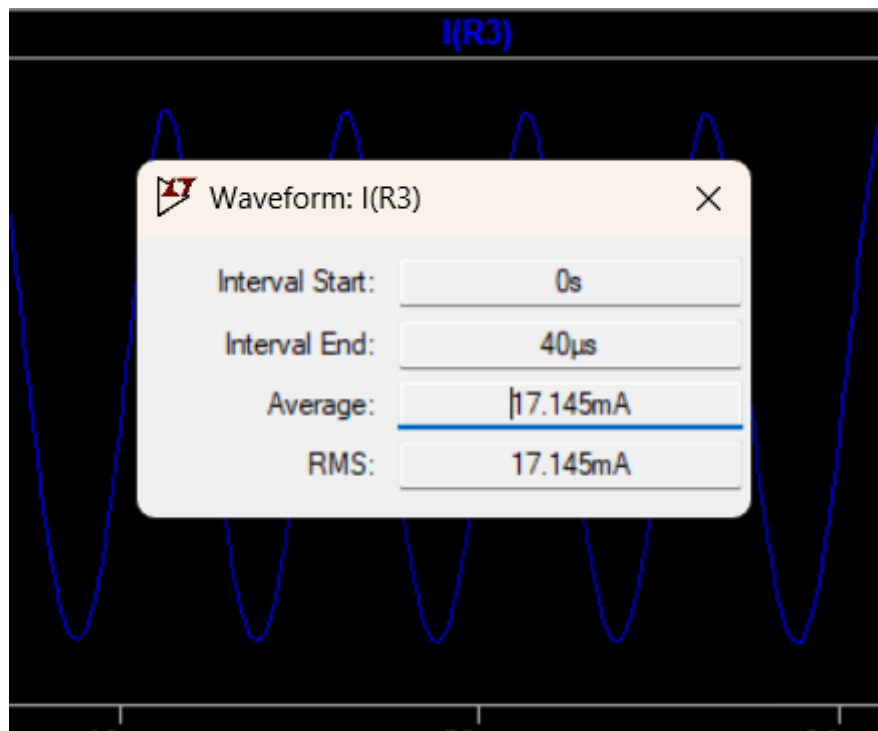


Fig. 4: Current of T1

 


Fig. 5: Current of T2

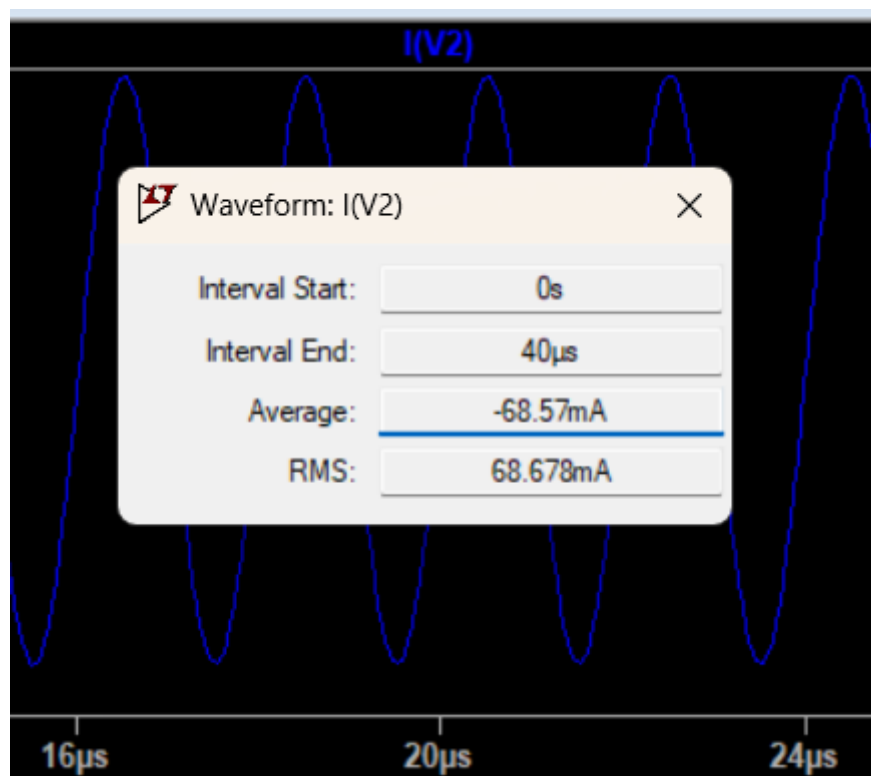


Fig. 6: Current consumption of the circuit

In methodology, collector current of T1 is chosen as 15mA, in analysis, it is measured as 17.1mA. Similarly, in methodology, collector current of T2 is chosen as 50mA, in analysis, it is measured as 49.1mA. Therefore, with a slight error included, desired results are obtained.

For the current consumption of the circuit, it is measured as 68.57mA, which is less than 70mA. So, first specification is satisfied.

## Second Specification:

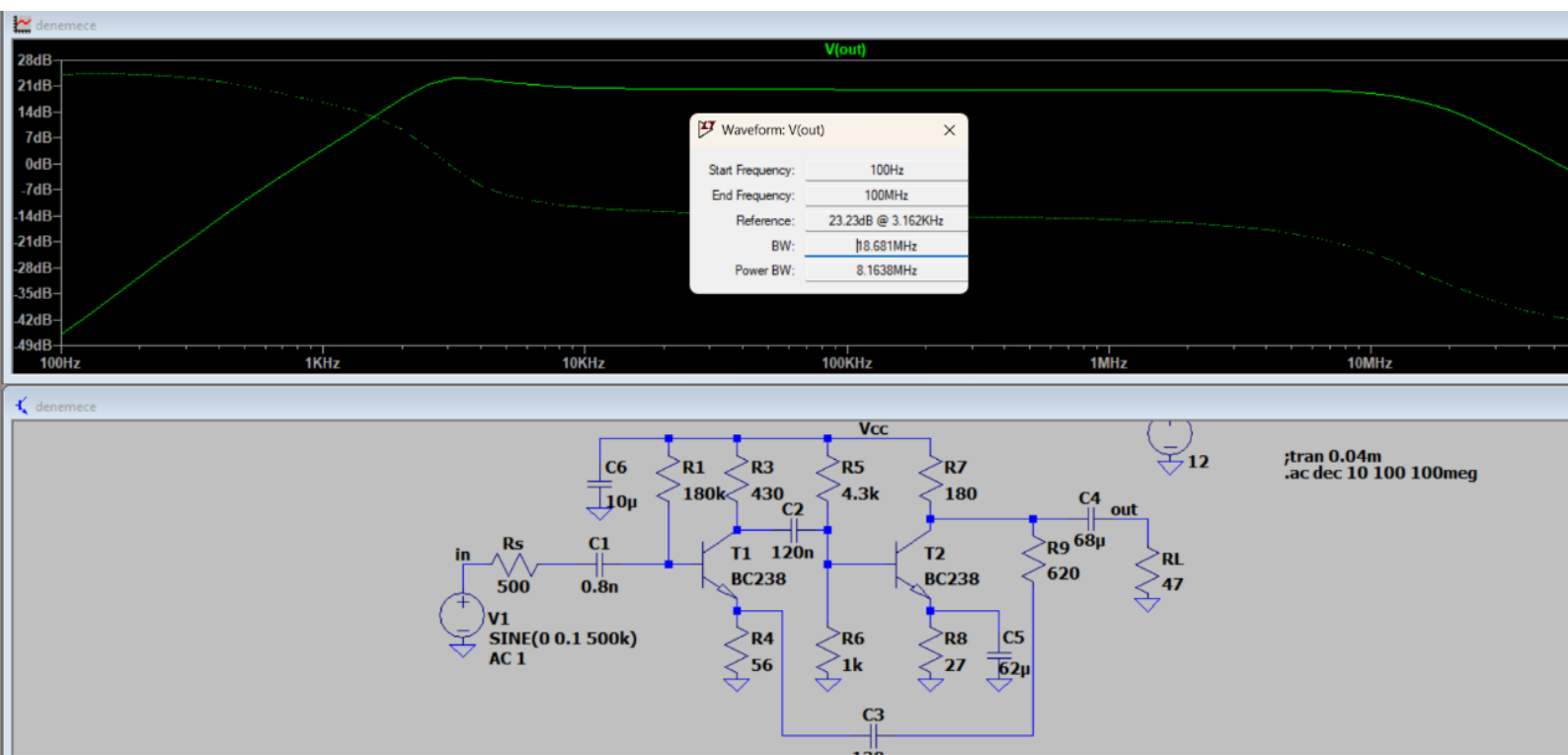


Fig. 7: BW of the designed circuit

Fig. 7 shows the bandwidth of the the designed circuit. BW is measured as 18.68MHz. -3dB points are 700Hz and 61.5MHz.

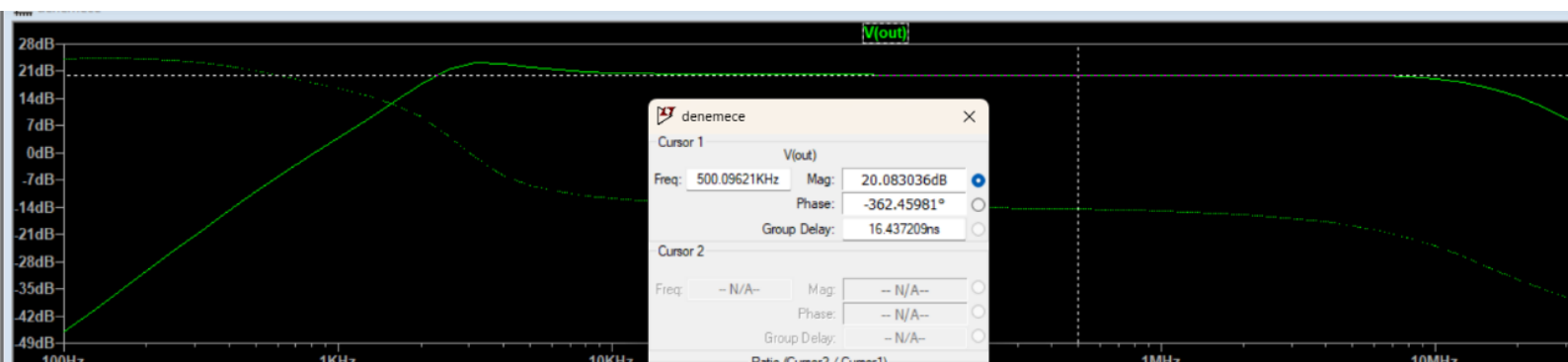


Fig. 8: dB gain at 500kHz

As seen from Fig. 8, at 500kHz, dB gain is 20.08, an gain is flat from 7kHz to 11MHz. Therefore second specification is also satisfied.

### Third Specification:

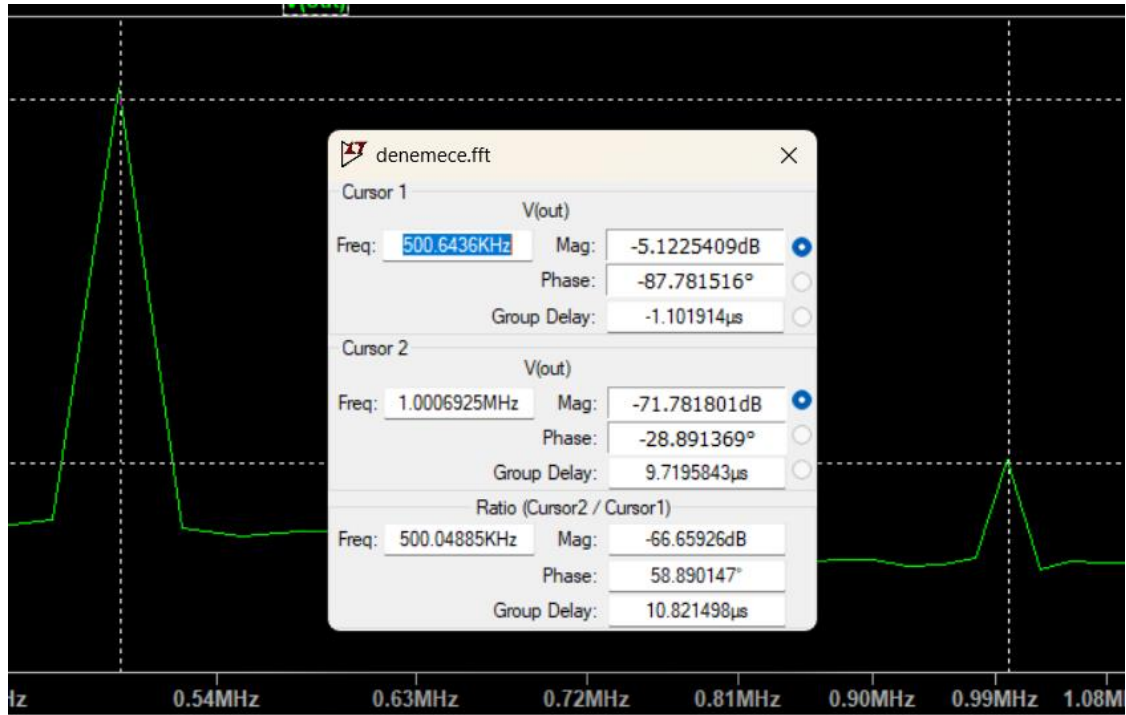


Fig. 9: dB difference between fundamental and second harmonic

Looking at the Fig. 9, dB gain at fundamental harmonic (500kHz) is -5.12 dB, at second harmonic, dB gain is -71.78 dB. The difference is -66.66dB, which is below -30dB. So, third and last specification is also satisfied.

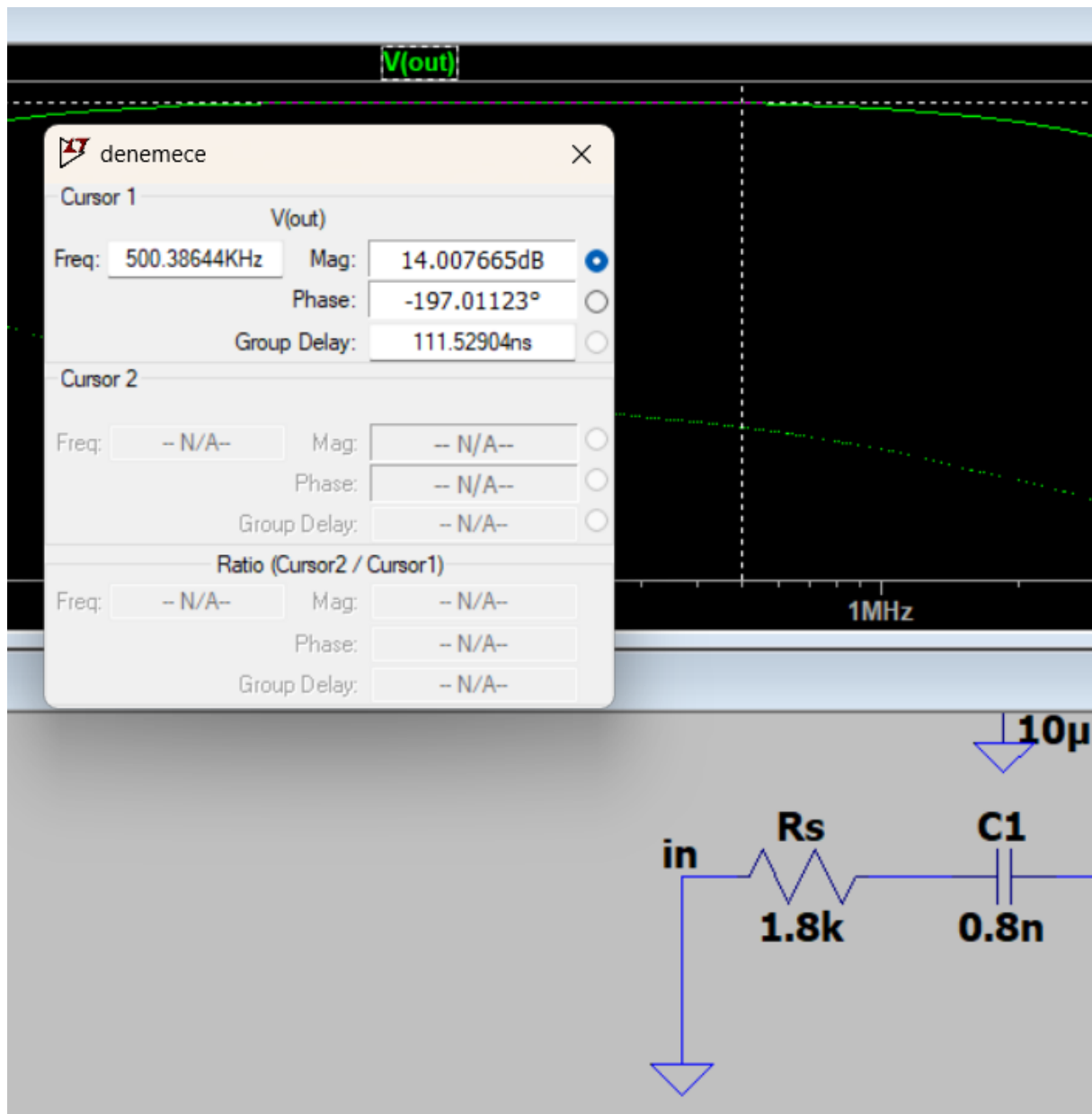


Fig. 10: Small signal input impedance value

I performed small signal AC analysis for the open-loop. Gradually increasing the value of  $R_s$  starting from  $1\Omega$ , I find the point where the dB gain is equal to 14dB. Fig. 10 shows that when  $R_s = 1.8k\Omega$ , dB gain equals to 14dB. Small signal input impedance of the circuit is  $1.8k\Omega$

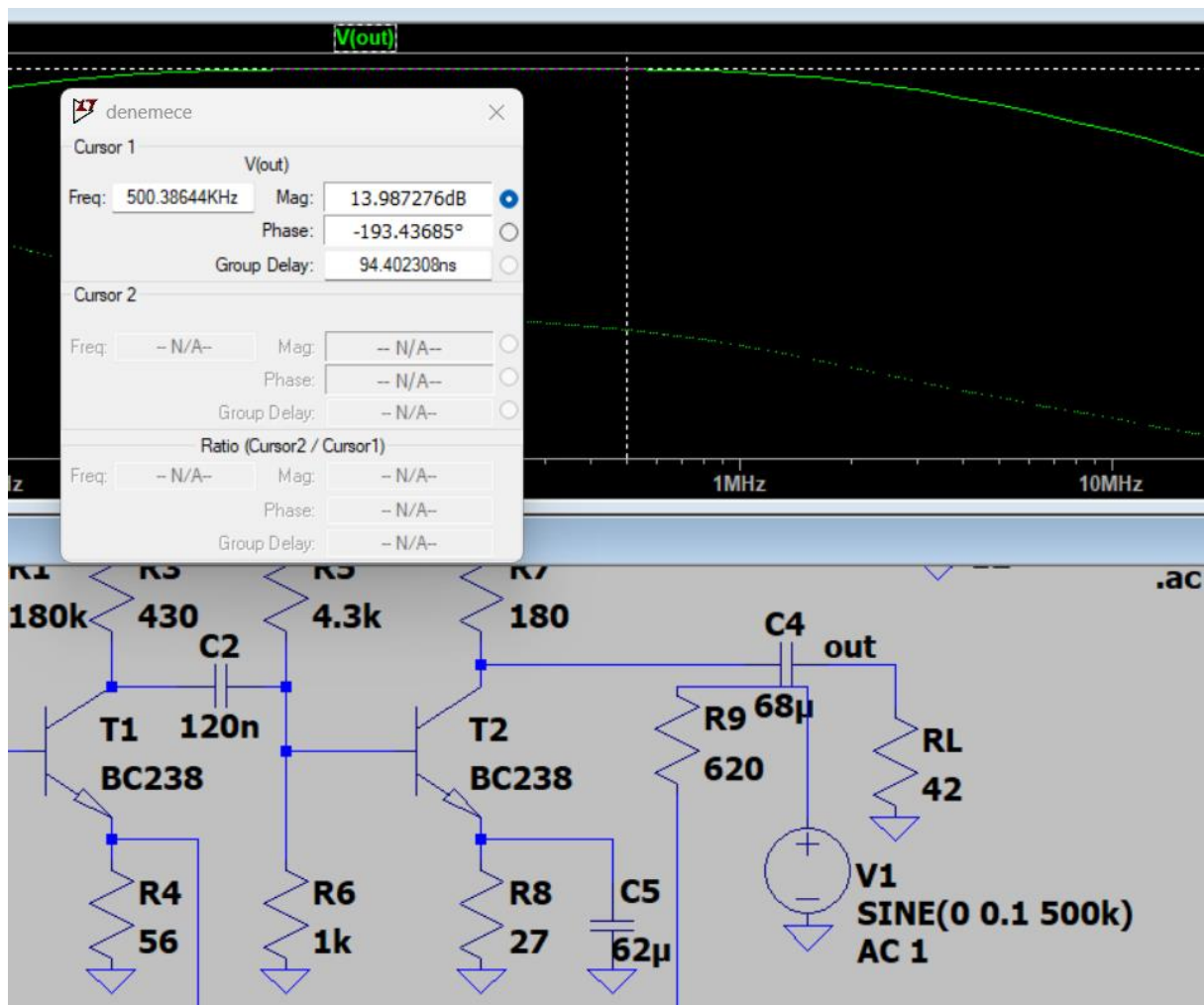


Fig. 11: Small signal input output value

Fig. 11 shows that when  $R_L$  value is  $42\Omega$ , dB gain is equal to  $13.99\text{dB}$ . So, small signal output impedance of the circuit is found as  $42\Omega$ .



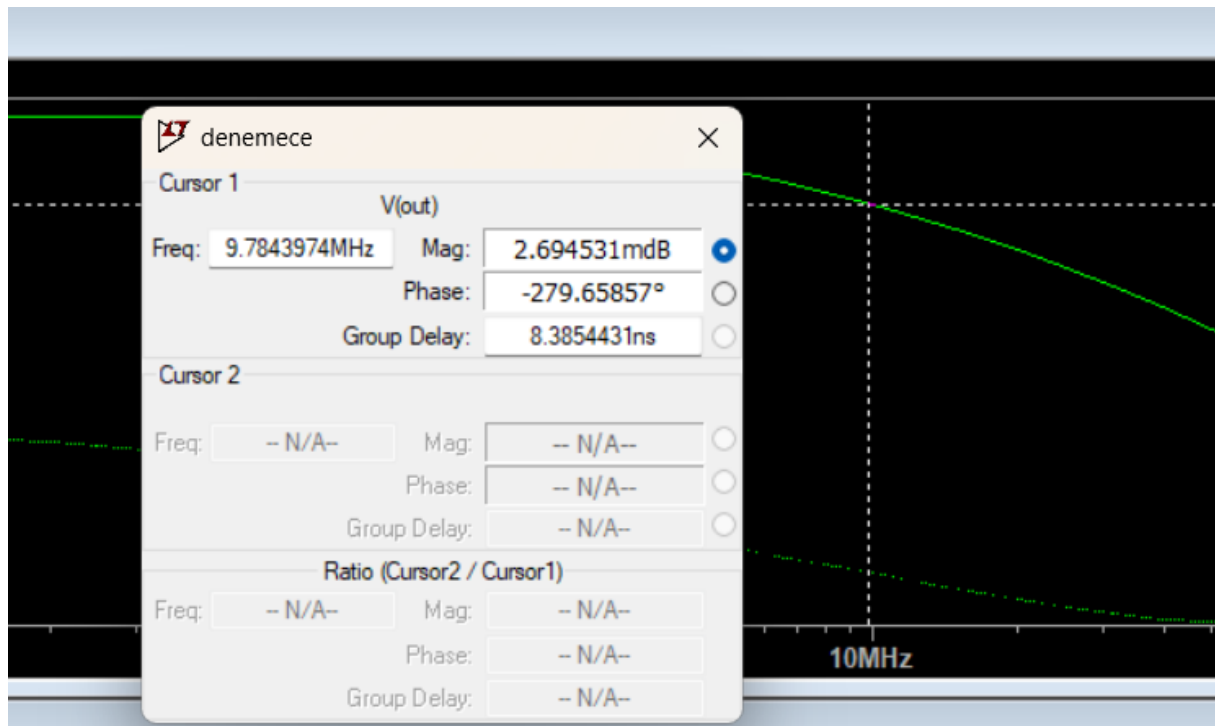


Fig. 12: Phase margin of the circuit

Looking at Fig. 12, phase margin of the circuit is calculated as  $-278 - (-360) = 82$  degree. It is greater than 45 degree, which is what is wanted.

DipTrace schematic of the circuit is given below.

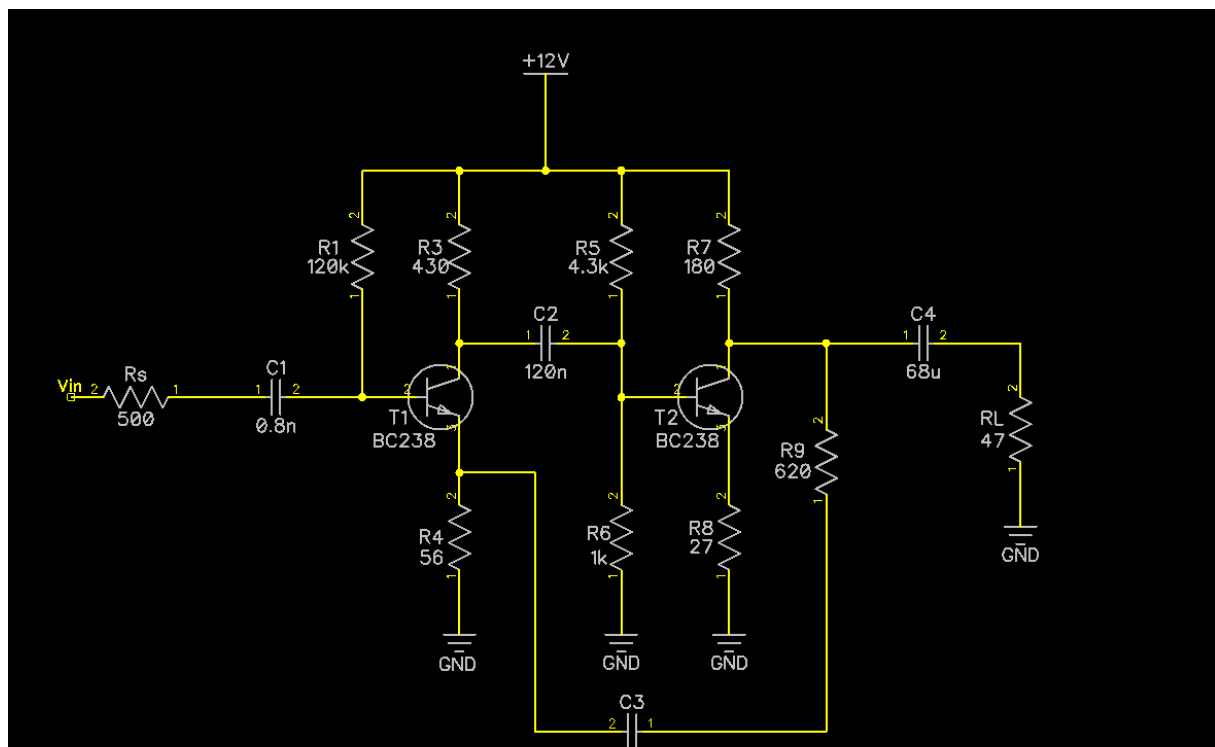


Fig. 13: DipTrace schematic

Fig. 14 shows the bill of materials.

#	RefDes	Value	Name	Quantity
1	C1, C2, C3, C4	0.8n	Capacitor, Polyester	4
2	R1, R3, R4, R5, R6, R7, R8, RL, Rs	120k	Resistor320	9
3	R9	620	Resistor420	1
4	T1, T2	BC238	BC238	2

*Fig. 14: Bill of Materials*